

VELLORE INSTITUTE OF TECHNOLOGY, VELLORE-632014
(Deemed to be University under section 3 of UGC Act, 1956)



VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

J Component Makethon Report on

“Design of Simple Processor”

Batch No : 3

MASTER OF TECHNOLOGY
in
VLSI DESIGN
FALL SEMESTER 2021-2022

Submitted by

Panchagnula Krishna Vamsidhar	21MVD0085
Shreyas S Bagi	21MVD0086
Pragya	21MVD0093
Suresh Bhati	21MVD0111
K Naga Sai Swaroop	21MVD0135

Under the guidance of

Dr. Nitish Kumar V
Associate Professor
School of Electronics Engineering(SENSE)
VIT, Vellore - 632014

SCHOOL OF ELECTRONICS ENGINEERING (SENSE)
2021-22

Chapter 1

Problem Statement and Problem Description

Design of Simple Processor Figure below shows a digital system that contains a number of 9-bit registers, a multiplexer, an adder/subtractor unit, and a control unit (finite state machine). Data is input to this system via the 9-bit DIN input. This data can be loaded through the 9-bit wide multiplexer into the various registers, such as R0, R7 and A. The multiplexer also allows data to be transferred from one register to another. The multiplexer's output wires are called a bus in the figure because this term is often used for wiring that allows data to be transferred from one location in a system to another. Addition or subtraction is performed by using the multiplexer to first place one 9-bit number onto the bus wires and loading this number into register A. Once this is done, a second 9-bit number is placed onto the bus, the adder/subtractor unit performs the required operation, and the result is loaded into register G. The data in G can then be transferred to one of the other registers as required.

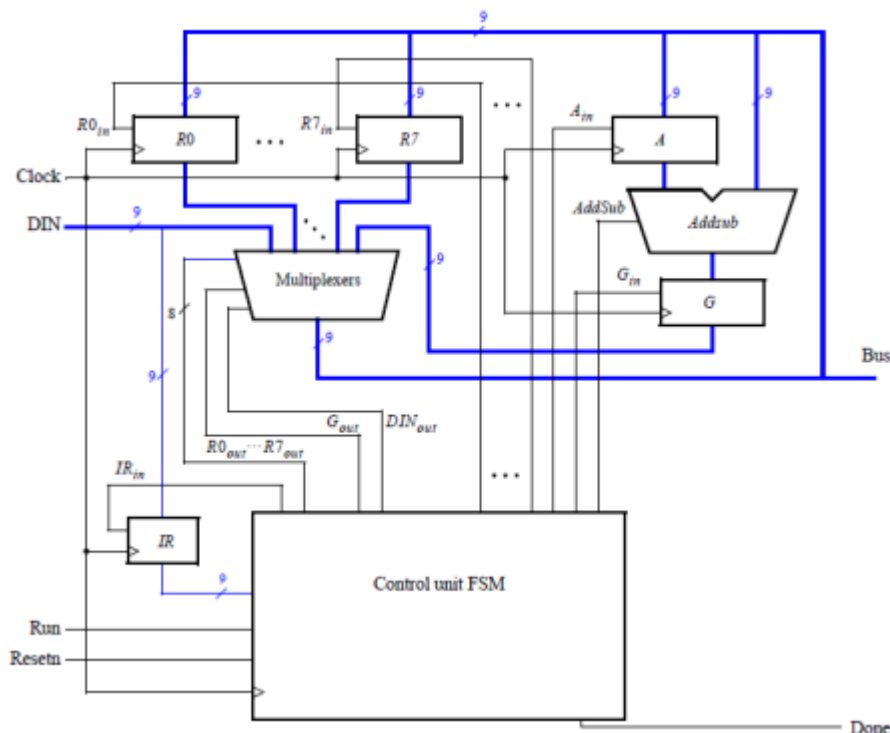


Figure 1.1 The Processor Block Diagram which includes Datapath and Control block separately.

The IR Register is of 9bit value and is loaded from DIN ate T0 state only.

IR[8:6]	IR[5:3]	IR[2:0]
---------	---------	---------

The IR[8:6] is encode with 000 has MOVE operation, 001 has ADD operation, 010 Subtraction operation and 011 Move Immediate operation.

The IR[5:3] and IR[2:0] is having encoding scheme like

000 R0 register

001 R1 register

010 R2 register

011 R3 register

100 R4 register

101 R5 register

110 R6 register

111 R7 register

Operation	Function performed
mv Rx, Ry	$Rx \leftarrow [Ry]$
mvi $Rx, \#D$	$Rx \leftarrow D$
add Rx, Ry	$Rx \leftarrow [Rx] + [Ry]$
sub Rx, Ry	$Rx \leftarrow [Rx] - [Ry]$

Figure 1.2 Operation of the Instruction

	T_1	T_2	T_3
(mv): I_0	$RY_{out}, RX_{in},$ <i>Done</i>		
(mvi): I_1	$DIN_{out}, RX_{in},$ <i>Done</i>		
(add): I_2	RX_{out}, A_{in}	RY_{out}, G_{in}	$G_{out}, RX_{in},$ <i>Done</i>
(sub): I_3	RX_{out}, A_{in}	$RY_{out}, G_{in},$ <i>AddSub</i>	$G_{out}, RX_{in},$ <i>Done</i>

Figure 1.3 Control Signals asserted in each Instruction/time step

Chapter 2

Block Diagram

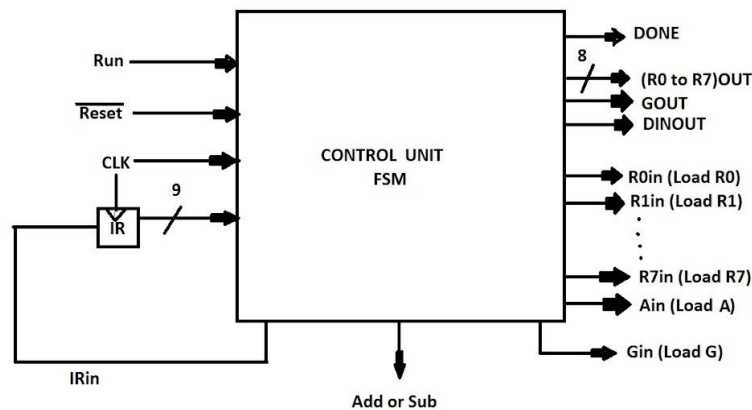


Figure 2.1 Operation of the Instruction : Block Diagram with respect to Control Unit FSM.

 


Figure 2.2 Block Diagram with respect to Datapath Unit.

The Datapath path consists of Mux, Adder or Subtractor and Control signal (like enable signals) from the Control Block FSM.

Verilog Code for Datapath Unit :

1. Adder or Subtractor Submodule

```

module adder_subtractor (LdA, LdG, Add_sub,data_in, clk,Z1);
input LdA, LdG, Add_sub,clk;
// Add_sub=1 add else subtract
// data_in is the output of the mux
input [8:0] data_in;
output reg [8:0] Z1;
reg [8:0] X1 ;
wire [8:0] X, Y, Z, Bus;
assign Bus = data_in;

always @ (posedge clk)
begin
X1 <= X;
Z1 <= Z;
end

// X is output of the Register A
PIPO1 A (X,Bus, LdA, clk);
//PIPO1 (dout, din, ld, clk);

// Y is output of the adder
// Adder block
add_sub h01 (Y, Bus,X, Add_sub);
//add_sub (out, in1, in2);

// Z is output of the Register G
PIPO1 B (Z,Y, LdG, clk);
//PIPO1 (dout, din, ld, clk);

endmodule

module PIPO1 (dout, din, ld, clk);
input [8:0] din;
input ld, clk;
output reg [8:0] dout;

always @ (posedge clk)
if (ld) dout <= din;

endmodule

module add_sub (out, in1, in2,Add_sub);
input [8:0] in1, in2;
output reg [8:0] out;
input Add_sub;
always @ (*)
begin
if (Add_sub)
out = in1 + in2;
else
out = in1-in2;
end
endmodule

```

Figure 2.3 Adder or Subtractor Submodule

```

module multiplex10_to_1 (Reg0in,Reg1in,Reg2in,Reg3in,Reg4in,Reg5in,Reg6in,Reg7in,DIn,G,sel,bus);
input  [8:0] Reg0in,Reg1in,Reg2in,Reg3in,Reg4in,Reg5in,Reg6in,Reg7in,DIn,G;
input  [9:0] sel;
//input Reg0out, Reg1out, Reg2out, Reg3out, Reg4out, Reg5out, Reg6out, Reg7out,Din_out,G_out;
output reg [8:0] bus;
always @ (sel or DIn or G)
begin
    if (sel == 10'b0000000001)
        bus <= DIn;
    else if (sel == 10'b0000000010)
        bus <= G;
    else if (sel == 10'b0000000100)
        bus <= Reg7in;
    else if (sel == 10'b0000001000)
        bus <= Reg6in;
    else if (sel == 10'b0000010000)
        bus <= Reg5in;
    else if (sel == 10'b0000100000)
        bus <= Reg4in;
    else if (sel == 10'b0001000000)
        bus <= Reg3in;
    else if (sel == 10'b0010000000)
        bus <= Reg2in;
    else if (sel == 10'b0100000000)
        bus <= Reg1in;
    else if (sel == 10'b1000000000)
        bus <= Reg0in;
    else
        bus <= bus;
end
endmodule

```

Figure 2.4 Multiplexer Module

```

module Reg_store(R0in, R1in,R2in,R3in,R4in,R5in,R6in,R7in,bus,R0,R1, R2, R3, R4, R5,R6, R7,clk);
input R0in, R1in,R2in,R3in,R4in,R5in,R6in,R7in;
input [8:0] bus;
input clk;
output reg [8:0] R0= 9'd0,R1= 9'd0, R2= 9'd0, R3= 9'd0, R4= 9'd0, R5= 9'd0,R6= 9'd0, R7 = 9'd0;

always @ (posedge clk)
begin
    if (R0in || R1in || R2in || R3in || R4in || R5in || R6in || R7in)
    begin
        if(R0in == 1)
            R0 <= bus;
        if (R1in == 1)
            R1 <= bus;
        if (R2in == 1)
            R2 <= bus;
        if (R3in == 1)
            R3 <= bus;
        if (R4in == 1)
            R4 <= bus;
        if (R5in == 1)
            R5 <= bus;
        if (R6in == 1)
            R6 <= bus;
        if (R7in == 1)
            R7 <= bus;
    end
    else
    begin
        R0 <= R0;
        R1 <= R1;
        R2 <= R2;
        R3 <= R3;
        R4 <= R4;
        R5 <= R5;
        R6 <= R6;
        R7 <= R7;
    end
end
endmodule

```

Figure 2.5 Register Module

```

module mux_add(R0in, R1in,R2in,R3in,R4in,R5in,R6in,R7in, DIn,sel, clk, R0,R1, R2, R3, R4, R5,R6, R7, LdA, LdG, Add_sub);
input R0in, R1in,R2in,R3in,R4in,R5in,R6in,R7in, LdA, LdG, Add_sub;
input [8:0] DIn;
output [8:0] R0,R1, R2, R3, R4, R5,R6, R7;
input [9:0] sel;
input clk;
wire [8:0] bus,G;
Reg_store ha2(R0in, R1in,R2in,R3in,R4in,R5in,R6in,R7in,bus,R0,R1, R2, R3, R4, R5,R6, R7,clk);
multiplex10_to_1 hal (R0,R1, R2, R3, R4, R5,R6, R7,DIn,G,sel,bus);
adder_subtractor g01 (LdA, LdG, Add_sub,bus, clk, G);
endmodule

```

Figure 2.6 Datapath Module with Control signals and Input for verifying the data path.

Simulation Output in Modelsim for the above operation

Note:

1. R0in to R7in are enable signals for registers Reg0 to Reg7;
2. Sel is a 10-bit input which represents selection inputs for the Multiplexer which represents control signals Sel[9:0]={Regout0, Regout1, Regout2, Regout3, Regout4, Regout5, Regout6, Regout7, Gout, Din(Data in) } respectively ;
3. R0 to R7 represents registers Reg0 to Reg7 & G represents Output Register of Alu, Bus register represents Data Bus;
4. LDA & LDG are enable control signals for A, G registers respectively, and clk represents clock signal;
5. Add_Sub is the control signal for adder/subtractor unit:
 - a. For Addition \Rightarrow Add_Sub=1
 - b. For Subtraction \Rightarrow Add_Sub=0

Datapath Verification:

 


Figure 2.7 Data taking

 


Figure 2.8 Assigning to the Bus

 


Figure 2.9 MVI Register

The IR Register is of 9bit value and is loaded from DIN at T0 state only.

 


Figure 2.10 Moving between R0 and R3

 


Figure 2.11 Subtracting R3 and R4 and storing in R4

 


Figure 2.12 Adding R3 and R4

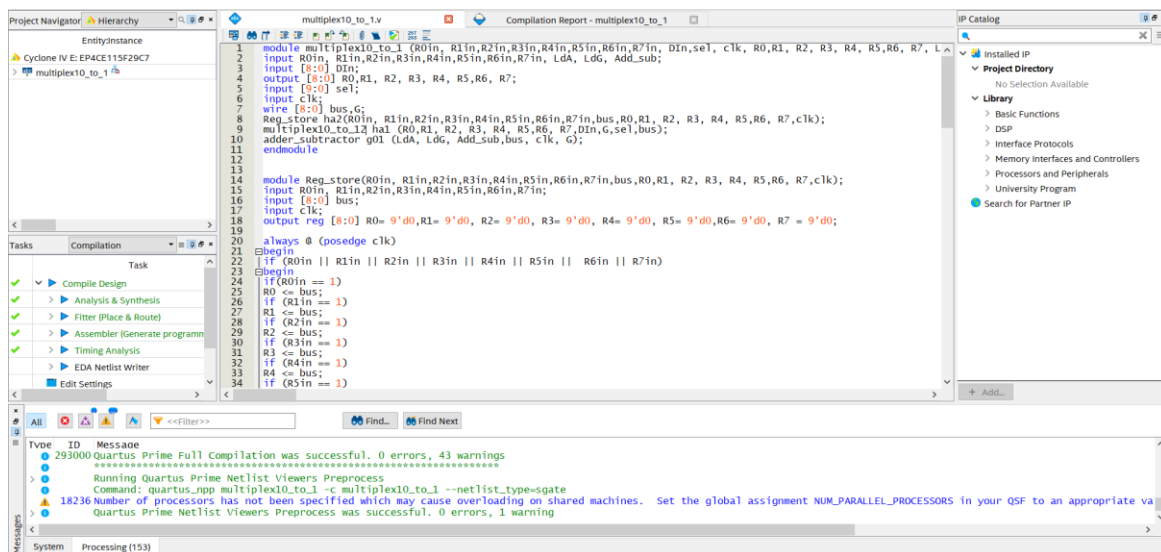


Figure 2.13 Quartus Prime Synthesis of the Datapath Module.

The Controller Path and Processor Integration Part:

```

1  module proc (DIN, Resetn, Clock, Run, Done, BusWires, Sel, LdR0, LdR1, LdR2, LdR3, LdR4, LdR5, LdR6, LdR7, LdA, LdG, Add_sub, Xreg, Yreg);
2  input [8:0] DIN;
3  input Resetn, Clock, Run;
4  output reg Done;
5  output [8:0] BusWires;
6  output reg [9:0] Sel;
7  output reg LdR0, LdR1, LdR2, LdR3, LdR4, LdR5, LdR6, LdR7, LdA, LdG, Add_sub;
8  output [9:0] Xreg, Yreg;
9  parameter T0 = 2'b00, T1 = 2'b01, T2 = 2'b10, T3 = 2'b11;
10 parameter mv = 3'b000, add = 3'b001, sub = 3'b010, mvi = 3'b011;
11
12 /*
13 mv R1,R2
14 000 001 010
15 */
16
17 reg Z=9'b111111111;
18 reg [1:0] PS,NS;
19
20 // Registers
21 reg [8:0] IRin;
22 //9'001001010;
23 reg [8:0] R0,R1,R2,R3,R4,R5,R6,R7; // 8 Internal Registers
24 reg [8:0] A,G; // Two registers

```

```

25
26 // T0 is for loading state
27 // If mv instruction then go T1 and RYout and LdRx enabled Control signals go high
28 // [8:0] IR
29 // [8,7,6] IR -----> Opcode
30 // [5,4,3] IR -----> RX
31 // [2,1,0] IR -----> RY
32 reg [2:0] opcode;
33 wire [8:0] Data_reg;
34 assign Data_reg = DIN;
35 // add R1,R2
36 //001 001 010 ----> Din at Time t=0
37 // State is in T0
38 //opcode = Data_reg [8:6];
39
40 reg En=1;
41
42 dec3to8 Z1 (IRin[5:3], En, Xreg);
43 // RX register
44 dec3to8 Z2 (IRin[2:0], En, Yreg);
45 // RY register

```

```

47  initial
48  begin
49      R0 = 9'b000000001;
50      R1 = 9'b000000010;
51      R2 = 9'b000000100;
52      R3 = 9'b000001000;
53      R4 = 9'b000010000;
54      R5 = 9'b000100000;
55      R6 = 9'b001000000;
56      R7 = 9'b010000000;
57      G  = 9'b111111111;
58  end
59
60  multiplex10_to_1 YZ1 (R0,R1,R2,R3,R4,R5,R6,R7,DIN,G,Sel,BusWires);
61  //mux_add G12 (LdR0,LdR1,LdR2,LdR3,LdR4,LdR5,LdR6,LdR7, DIN,Sel, Clock,LdA, LdG, Add_sub);
62
63  always @(posedge Clock)
64  begin
65      if(Resetn)
66          PS <= NS;
67      else
68          PS <= T0;
69  end

```

```

145      NS <= T1;
146      end
147      end
148  T2:begin
149      if(opcode == add)
150      begin
151          Sel <= Yreg;
152          LdA <= 0;
153          LdG <= 1;
154          G <= Z; // Z is result of addition from the adder block;
155          NS<=T3;
156      end
157
158      else if(opcode == sub)
159      begin
160          Sel <= Yreg;
161          LdA <= 0;
162          LdG <= 1;
163          G <= Z;
164          NS<=T3;
165      end
166      end
167  end

```

```

166     end
167
168
169 T3: begin
170     if(opcode == add)
171     begin
172         Done <= 1;
173         Sel<=10'b0000000010;
174         case(Xreg)
175             10'b1000000000: begin LdR0 <= 1; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R0 <= BusWires;end
176             10'b0100000000: begin LdR0 <= 0; LdR1 <= 1; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R1 <= BusWires;end
177             10'b0010000000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 1; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R2 <= BusWires;end
178             10'b0001000000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 1; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R3 <= BusWires;end
179             10'b0000100000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 1; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R4 <= BusWires;end
180             10'b0000010000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 1; LdR6 <= 0; LdR7 <= 0; R5 <= BusWires;end
181             10'b0000001000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 1; LdR7 <= 0; R6 <= BusWires;end
182             10'b0000000100: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 1; R7 <= BusWires; end
183         endcase
184     end
185
186     else if(opcode == sub)
187     begin
188         Done <= 1;
189         Sel<=10'b0000000010;
190         case(Xreg)
191             10'b1000000000: begin LdR0 <= 1; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R0 <= BusWires;end
192             10'b0100000000: begin LdR0 <= 0; LdR1 <= 1; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R1 <= BusWires;end
193             10'b0010000000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 1; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R2 <= BusWires;end
194             10'b0001000000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 1; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R3 <= BusWires;end
195             10'b0000100000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 1; LdR5 <= 0; LdR6 <= 0; LdR7 <= 0; R4 <= BusWires;end
196             10'b0000010000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 1; LdR6 <= 0; LdR7 <= 0; R5 <= BusWires;end
197             10'b0000001000: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 1; LdR7 <= 0; R6 <= BusWires;end
198             10'b0000000100: begin LdR0 <= 0; LdR1 <= 0; LdR2 <= 0; LdR3 <= 0; LdR4 <= 0; LdR5 <= 0; LdR6 <= 0; LdR7 <= 1; R7 <= BusWires;end
199         endcase
200     end
201 end

```

Activate Windows
Go to Settings to activate Windows.

```

199     endcase
200     end
201 end
202
203 default : NS<=T0;
204 endcase
205 end
206
207 endmodule
208
209 module dec3to8(W, En, Y);
210     input [2:0] W;
211     input En;
212     output reg [9:0] Y;
213
214     always @(W or En)
215     begin
216         if (En == 1)
217         case (W)
218             3'b000: Y = 10'b1000000000;
219             3'b001: Y = 10'b0100000000;
220             3'b010: Y = 10'b0010000000;
221             3'b011: Y = 10'b0001000000;
222             3'b100: Y = 10'b0000100000;
223             3'b101: Y = 10'b0000010000;
224             3'b110: Y = 10'b0000001000;
225             3'b111: Y = 10'b0000000100;
226             //3'b1000: Y = 10'b0000000010;
227         endcase

```

```

226 //3'b1000: Y = 10'b0000000010;
227 endcase
228 else
229 Y = 10'b1000000000;
230 end
231 endmodule
232 module multiplex10_to_1 (Reg0in,Reg1in,Reg2in,Reg3in,Reg4in,Reg5in,Reg6in,Reg7in,DIn,G,sel,bus);
233 input [8:0] Reg0in,Reg1in,Reg2in,Reg3in,Reg4in,Reg5in,Reg6in,Reg7in,DIn,G;
234 input [9:0] sel;
235 //input Reg0out, Reg1out, Reg2out, Reg3out, Reg4out, Reg5out, Reg6out, Reg7out,Din_out,G_out;
236 output reg [8:0] bus;
237 always @ (sel or DIn or G)
238 begin
239     if (sel == 10'b0000000001)
240         bus <= DIn;
241     else if (sel == 10'b0000000010)
242         bus <= G;
243     else if (sel == 10'b0000000100)
244         bus <= Reg7in;
245     else if (sel == 10'b0000001000)
246         bus <= Reg6in;
247     else if (sel == 10'b0000010000)
248         bus <= Reg5in;
249     else if (sel == 10'b0000100000)
250         bus <= Reg4in;
251     else if (sel == 10'b0001000000)
252         bus <= Reg3in;
253     else if (sel == 10'b0010000000)
254         bus <= Reg2in;
255     else if (sel == 10'b0100000000)
256         bus <= Reg1in;
257     else if (sel == 10'b1000000000)
258         bus <= Reg0in;
259     else
260         bus <= bus;
261 end
262 endmodule

```

Testbench Code

```

1 module testbench_proc();
2 reg [8:0] DIN;
3 reg Resetn, Clock, Run;
4 wire Done;
5 wire[8:0] BusWires;
6 wire [9:0] Sel,Xreg, Yreg;
7 wire LdR0,LdR1,LdR2,LdR3,LdR4,LdR5,LdR6,LdR7,LdA,LdG,Add_sub;
8
9 proc X1 (DIN, Resetn, Clock, Run, Done, BusWires, Sel,LdR0,LdR1,LdR2,LdR3,LdR4,LdR5,LdR6,LdR7,LdA,LdG,Add_sub,Xreg, Yreg);
10
11 initial
12 begin
13     Clock = 1'b0;
14     Resetn = 1'b1;
15     Run = 0;
16     #1 Run = 1;
17     #100 $finish;
18 end
19
20 always #5 Clock = ~ Clock;
21
22 initial
23 begin
24     $monitor($time,"Clock=%b, Resetn=%b, Run=%b, DIN=%b, IRin=%b,Done=%b, BusWires=%b, LdR0=%b,LdR1=%b,LdR2=%b,LdR3=%b,
25         LdR4=%b,LdR5=%b,LdR6=%b,LdR7=%b,LdA=%b,LdG=%b,Add_sub=%b,PS=%b,NS=%b,opcode=%b",Clock,Resetn,Run,DIN,testbench_proc.X1.
26         IRin,Done,BusWires,LdR0,LdR1,LdR2,LdR3,LdR4,LdR5,LdR6,LdR7,LdA,LdG,Add_sub, testbench_proc.X1.PS,testbench_proc.X1.NS,testbench_proc.X1.opcode);
27 end
28
29 initial
30 begin
31     #1 DIN = 9'b001001010;
32 end
33
34 endmodule

```

The DIN is provided as Input and Loaded to IRin Register in T0 state only.

Move Operation

In Testbench we are Loading DIN=9'000001010. At T0 state only DIN is loaded to IRin Register and opcode = IRin[8:6], XReg = IRin[5:3] and YReg = IRin[2:0]. Here, XReg and YReg are used for Decoding the registers.

In this screenshot at t=0.005ns the T0 state is considered. So, IRin=9'b000001010 so, 000 --- Move, 001 --- R1 and 010 --- R2. Loading the data from R2 to R1. Here, we have predefined the values of R0 to R1 initial values. At T1 state according to the table here RYout corresponds to Select line for Mux and RXin is corresponding to the Load signal or Enable signal generated from the ControlFSM Block.

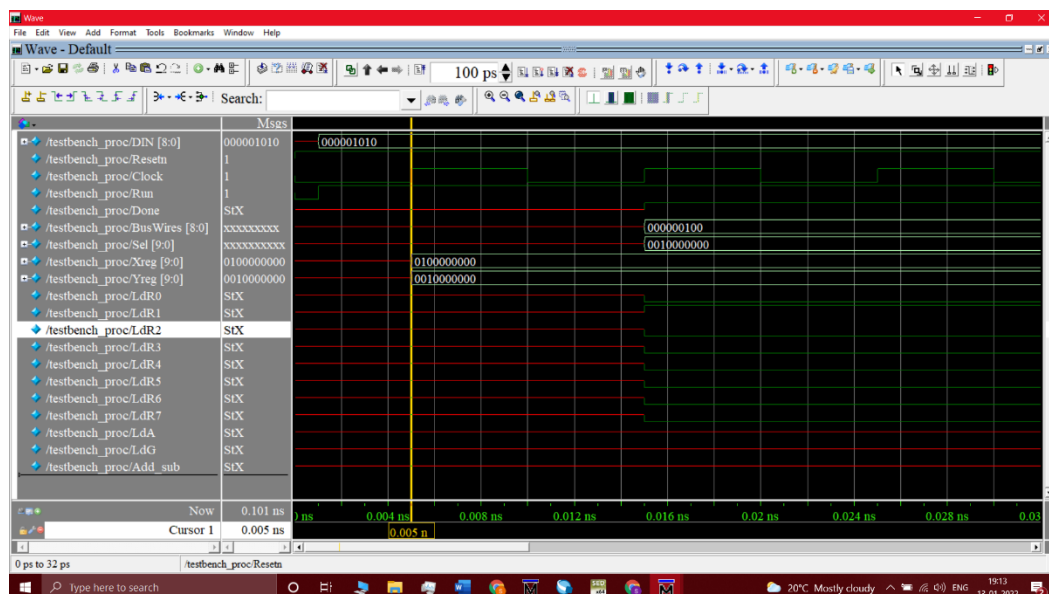


Figure 2.14 T0 state for Move operation.

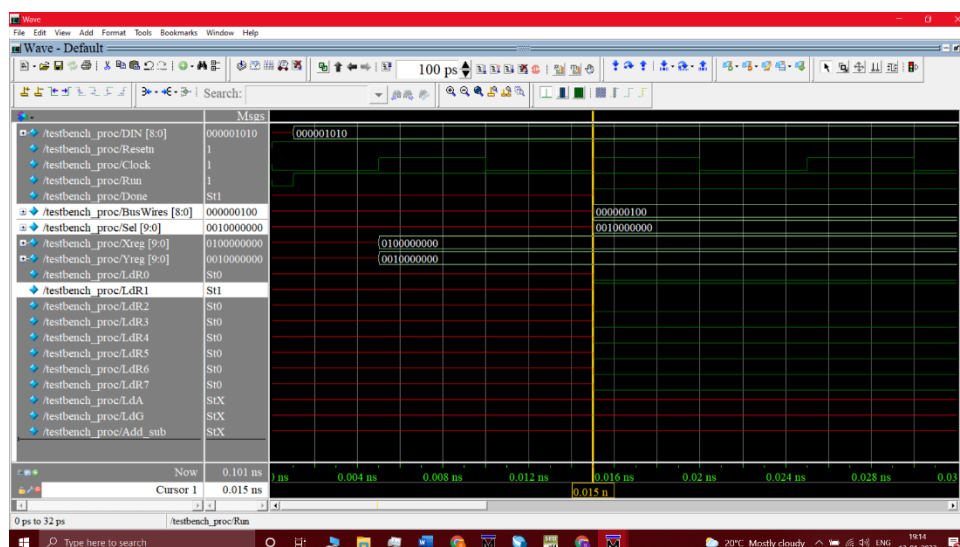


Figure 2.15 T1 state for Move operation. The BusWires lines is loaded with data stored in R2 and LdR1 signal is asserted high. So, the data is stored to R1 register.

Adder Operation

In Testbench we are Loading DIN=9'00100 010. At T0 state only DIN is loaded to IRin Register and opcode = IRin[8:6], XReg = IRin[5:3] and YReg = IRin[2:0]. Here, XReg and YReg are used for Decoding the registers.

In this screenshot at t=0.005ns the T0 state is considered. So, IRin=9'b001001010 so, 001 --- Add, 001 --- R1 and 010 --- R2. Add R1 and R2 and store back to R1. Here, we have predefined the values of R0 to R1 initial values.

 


Figure 2.16 Adder operation at T0 state. IRin is loaded with DIN.

```
# 0Clock=0, Resetn=1, Run=0, DIN=xxxxxxx,IRin=xxxxxxx,Done=x, BusWires=xxxxxxx, LdR0=x,LdR1=x,LdR2=x,
LdR3=x,LdR4=x,LdR5=x,LdR6=x,LdR7=x,LdA=x,LdG=x,Add_sub=x,PS=xx,NS=00,opcode=xxx
# 1Clock=0, Resetn=1, Run=1, DIN=001001010,IRin=xxxxxxx,Done=x, BusWires=xxxxxxx, LdR0=x,LdR1=x,LdR2=x,
LdR3=x,LdR4=x,LdR5=x,LdR6=x,LdR7=x,LdA=x,LdG=x,Add_sub=x,PS=xx,NS=00,opcode=xxx
# 5Clock=1, Resetn=1, Run=1, DIN=001001010,IRin=001001010,Done=x, BusWires=xxxxxxx, LdR0=x,LdR1=x,LdR2=x,
LdR3=x,LdR4=x,LdR5=x,LdR6=x,LdR7=x,LdA=x,LdG=x,Add_sub=x,PS=00,NS=01,opcode=001
# 10Clock=0, Resetn=1, Run=1, DIN=001001010,IRin=001001010,Done=x, BusWires=xxxxxxx, LdR0=x,LdR1=x,LdR2=x,
LdR3=x,LdR4=x,LdR5=x,LdR6=x,LdR7=x,LdA=x,LdG=x,Add_sub=x,PS=00,NS=01,opcode=001
```

Figure 2.17 At 5ns we observe the loading the operation part.

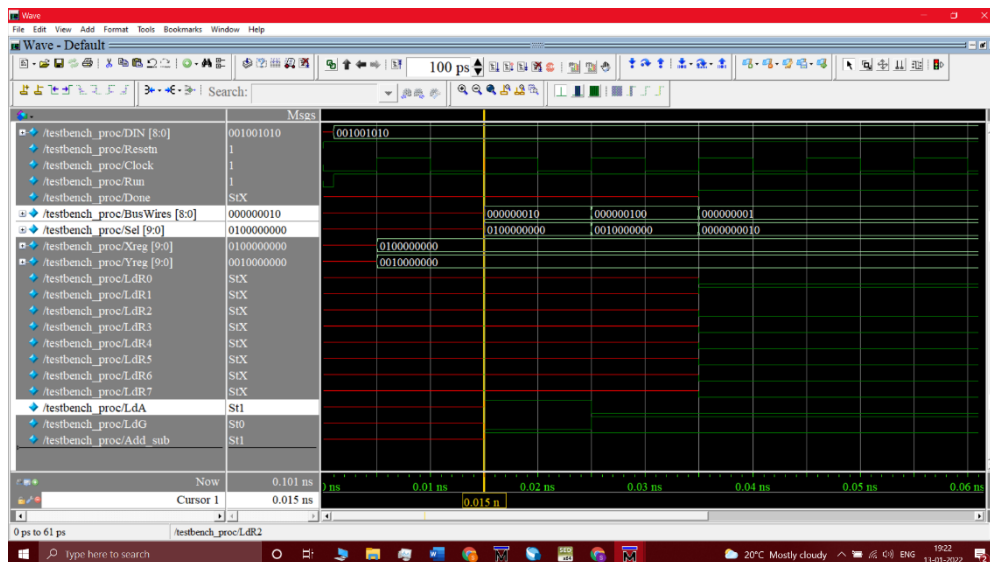


Figure 2.18 Adder operation at T1 state. Here, The LdA signal asserted high, so now the data stored from R1 (The select line for R1 is 0100000000) is written to A register. We are setting Add Sub =1 for adder operation and Add-Sub = 0 for subtraction.

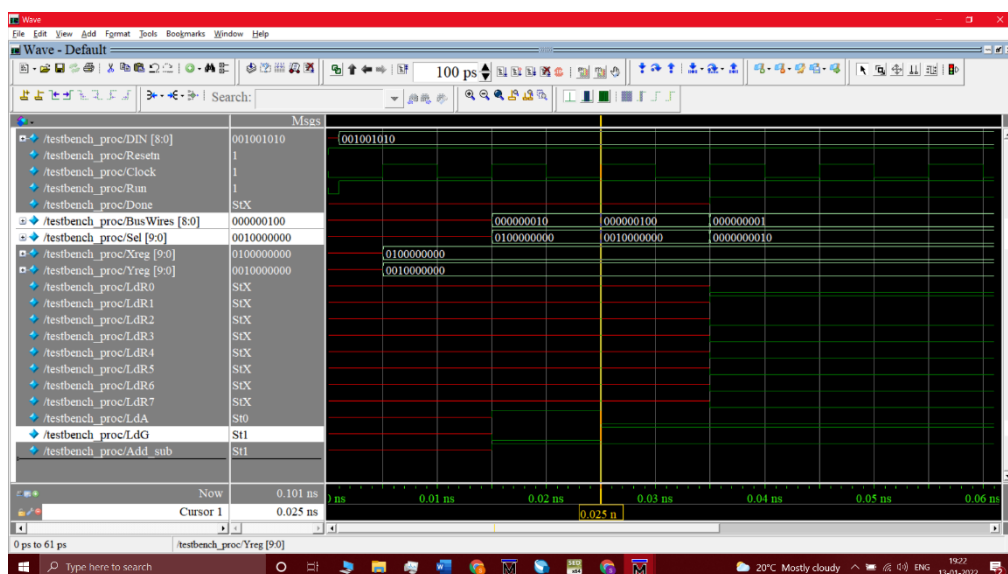


Figure 2.19 Adder Operation at T2 state.

Since the Adder or subtractor block is combinational block, it will be continuously adding. Here, at 25ns the LdG is asserted High and the R2 value is loaded to Adder with A register output signal to adder and saved in G register.

Here, we have implemented Control Path and Datapath separately integration part we have not done. So, In T3 state the data stored in G is loaded back to R1 through Mux by selecting the Select line of R1 register.

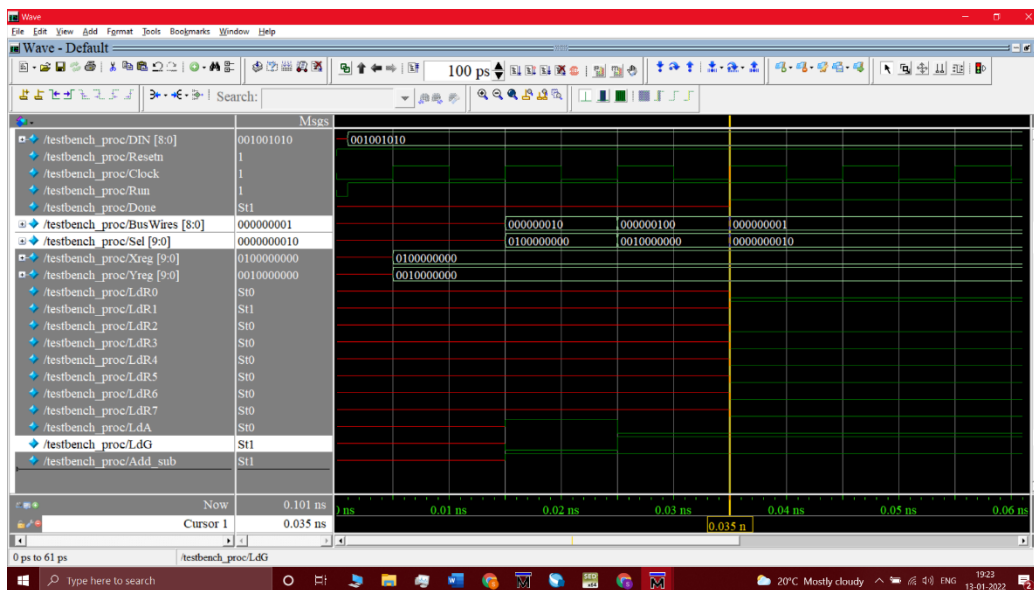


Figure 2.20 Adder Operation at T3 state.

Since, as said we did not integrate Dataflow and Controller Block, so the G register is loaded with predefined value and LdR1 is made high. So, now the BusWires is output of Mux and Loaded to R1. Similarly, for Subtraction Operation In T1 state Add Sub control signal will be 0. The Figure 2.21 will show its working.

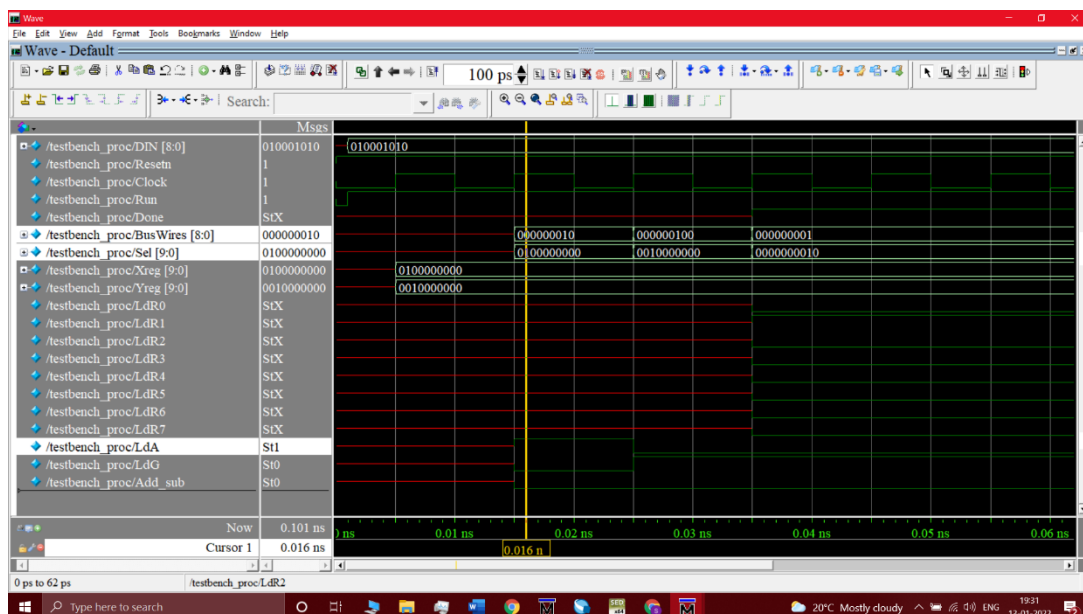


Figure 2.21 Subtraction Operation at T3 state. See the Add_sub control signal is 0.

Move Immediate Operation :

In Testbench we are Loading DIN=9' b011010011. At T0 state only DIN is loaded to IRin Register and opcode = IRin[8:6], XReg = IRin[5:3] and YReg = IRin[2:0]. Here, XReg and YReg are used for Decoding the registers.

In this screenshot at t=0.005ns the T0 state is considered. So, IRin=9'b000001010 so, 011 --- Move Immediate, 010 --- R2 and YYY part of register has no importance. Loading the data from DIN to R2 only at the next clock cycle after decoding. Here, we have predefined the values of R0 to R1 initial values.

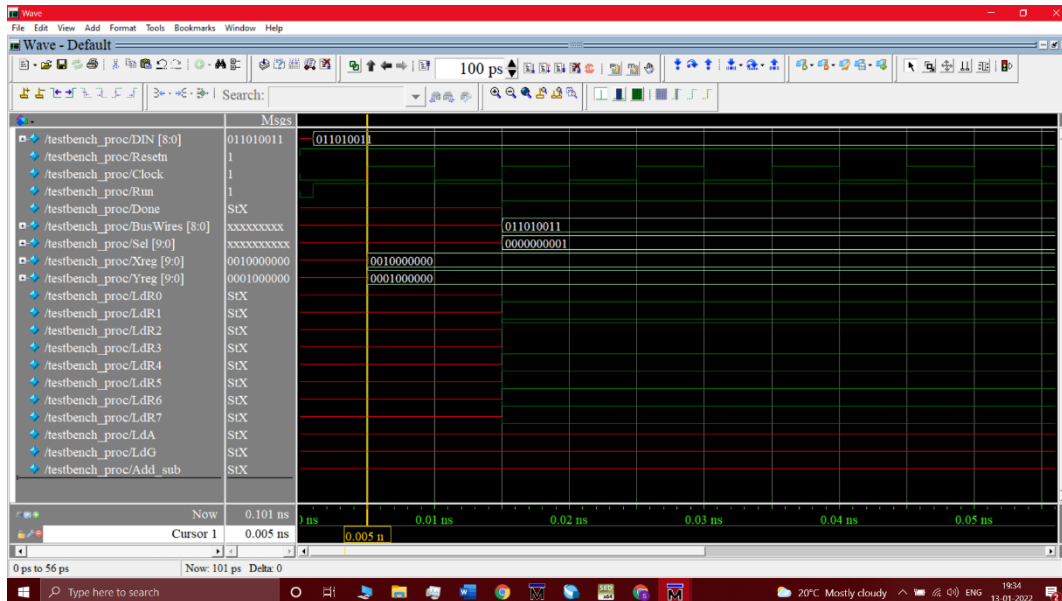


Figure 2.22 T0 state for Move Immediate operation. Instruction decoding takes place.

Result :

The Processor Controller Path and Datapath is implemented in Modelsim and Verified. The Control signal are generated from the Controller block and Datapath is able to load data based on Control signal